


Input			Output	
a	b	cin	result	cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0

1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

➔  $\text{result} = a \wedge b \wedge \text{cin}$   
 $\text{cout} = (a \& b) \mid (a \& \text{cin}) \mid (b \& \text{cin})$

### ➤ ALU

I use the behavioral 32-bit ALU from the textbook directly.

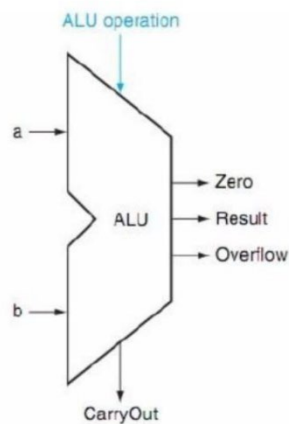


**FIGURE C.5.14** The symbol commonly used to represent an ALU, as shown in Figure C.5.12. This symbol is also used to represent an adder, so it is normally labeled either with ALU or Adder.

### ➤ MUX\_2to1

The function of this module is to choose one data from the given two data. So the output depends on how “select\_i” specifies and chooses the corresponding data.

 
### ➤ Shift\_Left\_Two\_32

Every bit shifts left by two bits, with the last two lsb given 0s.


 
### ➤ Sign\_Extend

Bit 16~31 are the duplicate of msb of the input, while the remaining bits are the same as the input.



### ➤ ALU\_Ctrl

	Input									Output			
	fc5	fc4	fc3	fc2	fc1	fc0	op2	op1	op0	ctr3	ctr2	ctr1	ctr0
add	1	0	0	0	0	0	1	1	0	0	0	1	0
sub	1	0	0	0	1	0	1	1	0	0	1	1	0
and	1	0	0	1	0	0	1	1	0	0	0	0	0
or	1	0	0	1	0	1	1	1	0	0	0	0	1
slt	1	0	1	0	1	0	1	1	0	0	1	1	1
jr	0	0	1	0	0	0	1	1	0	0	0	0	0
addi	x	x	x	x	x	x	0	0	0	0	0	1	0
slti	x	x	x	x	x	x	1	0	1	0	1	1	1
beq	x	x	x	x	x	x	0	0	1	0	1	1	0
lw	x	x	x	x	x	x	0	0	0	0	0	1	0
sw	x	x	x	x	x	x	0	0	0	0	0	1	0
jp	x	x	x	x	x	x	x	x	x	x	x	x	x
jal	x	x	x	x	x	x	x	x	x	x	x	x	x

given function field

ALU opcode  
designed by me

ALU control

➔  $ctr3 = 0$

$ctr2 = (fc1 \& op1) | op0$

$ctr1 = (fc5 \& \sim fc2) | (\sim op1)$

$ctr0 = (fc2 \& fc0 \& op1) | (fc3 \& fc1 \& op1) | (op2 \& op0)$

## ➤ Decoder

	Input						Output						
	op5	op4	op3	op2	op1	op0	RW	alu op2	alu op1	alu op0	Src	RD	Brh
R-f	0	0	0	0	0	0	1	1	1	0	0	01	0
addi	0	0	1	0	0	0	1	0	0	0	1	00	0
slti	0	0	1	0	1	0	1	1	0	1	1	00	0
beq	0	0	0	1	0	0	0	0	0	1	0	xx	1
lw	1	0	0	0	1	1	1	0	0	0	1	00	0
sw	1	0	1	0	1	1	0	0	0	0	1	xx	0
jp	0	0	0	0	1	0	0	x	x	x	x	xx	0
jal	0	0	0	0	1	1	1	x	x	x	x	10	0

given op field      RegWrite      ALU opcode designed by me      ALUSrc      RegDst      Branch

➔  $RW = (\sim op3 \& op1 \& op0) \mid (op3 \& \sim op0) \mid (\sim op3 \& \sim op2 \& \sim op1)$   
 $alu\_op2 = (\sim op3 \& \sim op2 \& \sim op1) \mid (\sim op2 \& op1 \& \sim op0)$   
 $alu\_op1 = \sim op3 \& \sim op2 \& \sim op1$   
 $alu\_op0 = \sim op5 \& (op2 \mid op1)$   
 $Src = op5 \mid op3$   
 $RD[1] = \sim op5 \& op0$   
 $RD[0] = \sim op3 \& \sim op2 \& \sim op1$   
 $Brh = op2$

	Input						Output			
	op5	op4	op3	op2	op1	op0	jump	memread	memwr	memto
R-f	0	0	0	0	0	0	0	0	0	00
addi	0	0	1	0	0	0	0	0	0	00
slti	0	0	1	0	1	0	0	0	0	00
beq	0	0	0	1	0	0	0	0	0	xx
lw	1	0	0	0	1	1	0	1	0	01
sw	1	0	1	0	1	1	0	0	1	xx
jp	0	0	0	0	1	0	1	0	0	xx
jal	0	0	0	0	1	1	1	0	0	10

given op field      Jump      MemRead      MemWrite      MemtoReg

➔  $\text{jump} = \sim\text{op5} \ \& \ \sim\text{op3} \ \& \ \text{op1}$   
 $\text{memread} = \text{op5} \ \& \ \sim\text{op3}$   
 $\text{memwr} = \text{op5} \ \& \ \text{op3}$   
 $\text{memto}[1] = \sim\text{op5} \ \& \ \text{op0}$   
 $\text{memto}[0] = \text{op5} \ \& \ \sim\text{op3}$

### ➤ MUX\_3to1

Similar to MUX\_2to1. The difference is that there are three data to choose from, so “select\_i” should be two bits.

### ➤ Simple\_Single\_CPU

By reference to the architecture diagram, include all the required modules, and carefully connect the wires between them, done!

Some special wires:

{	✓ $\text{jr\_ctr} = (\text{ALU\_op}[2] \ \& \ \text{ALU\_op}[1] \ \& \ \sim\text{ALU\_op}[0]) \ \& \ (\sim\text{instr\_o}[5] \ \& \ \sim\text{instr\_o}[4] \ \& \ \text{instr\_o}[3] \ \& \ \sim\text{instr\_o}[2] \ \& \ \sim\text{instr\_o}[1] \ \& \ \sim\text{instr\_o}[0])$ ➔ 1, if the instruction is jr ✓ $\text{nextAdd} = \text{branch} \ \& \ \text{zero}$ ➔ 1, if the instruction is branch ✓ $\text{jumpAdd} = \{ \text{seqAdd}[31:28], \text{jumpAdd\_tmp}[27:0] \}$ ➔ $\{ \text{PC}[31:28], \text{address} \ll 2 \}$
---	---

## Finished part:

### ✓ test data1

The instructions do some addition among the registers, store r1 and r2 to the memory, and load the values from the memory back to r6, r7, and r9. We see that the results are correct. r29 represents the stack pointer register value, that is, 128.

r0=	0	m0=	1
r1=	1	m1=	2
r2=	2	m2=	0
r3=	3	m3=	0
r4=	4	m4=	0
r5=	5	m5=	0
r6=	1	m6=	0
r7=	2	m7=	0
r8=	4	m8=	0
r9=	2	m9=	0
r10=	0	m10=	0
r11=	0	m11=	0
r12=	0	m12=	0
r13=	0	m13=	0
r14=	0	m14=	0
r15=	0	m15=	0
r16=	0	m16=	0
r17=	0	m17=	0
r18=	0	m18=	0
r19=	0	m19=	0
r20=	0	m20=	0
r21=	0	m21=	0
r22=	0	m22=	0
r23=	0	m23=	0
r24=	0	m24=	0
r25=	0	m25=	0
r26=	0	m26=	0
r27=	0	m27=	0
r28=	0	m28=	0
r29=	128	m29=	0
r30=	0	m30=	0
r31=	0	m31=	0

### ✓ test data2

This is a Fibonacci function looking for the fifth number in Fibonacci sequence ( f(4) ). The answer is stored in r2, and we see that “5” is the correct answer.

r0=	0	m0=	0
r1=	0	m1=	0
r2=	5	m2=	0
r3=	0	m3=	0
r4=	0	m4=	0
r5=	0	m5=	0
r6=	0	m6=	0
r7=	0	m7=	0
r8=	0	m8=	0
r9=	1	m9=	0
r10=	0	m10=	0
r11=	0	m11=	0
r12=	0	m12=	0
r13=	0	m13=	0
r14=	0	m14=	0
r15=	0	m15=	0
r16=	0	m16=	0
r17=	0	m17=	0
r18=	0	m18=	0
r19=	0	m19=	0
r20=	0	m20=	68
r21=	0	m21=	2
r22=	0	m22=	1
r23=	0	m23=	68
r24=	0	m24=	2
r25=	0	m25=	1
r26=	0	m26=	68
r27=	0	m27=	4
r28=	0	m28=	3
r29=	128	m29=	16
r30=	0	m30=	0
r31=	16	m31=	0

### **Problems you met and solutions:**

At first I couldn't get the correct answer for Fibonacci function, the result of r2 was very large. Since I had no problem for test data1, I guessed there was something wrong with my "jal" or "jr".

I looked for the introduction to these two instructions on the Internet, and found that I misunderstood the function of "jr", I assigned it a wrong "ALUCtrl\_o" code. So the solution was to revise the truth table, then I could get the correct answer.

### **Summary:**

This lab was similar to the previous one. However, I had a hard time implementing it. It was mainly due to my ambiguous understanding of the function of "jump", "jal", and "jr". I spent some time trying to realize those instructions, and found they should be nothing difficult at all.

Anyway, starting with some simple units, and implement a complete single cycle CPU step by step gave me a sense of achievement!